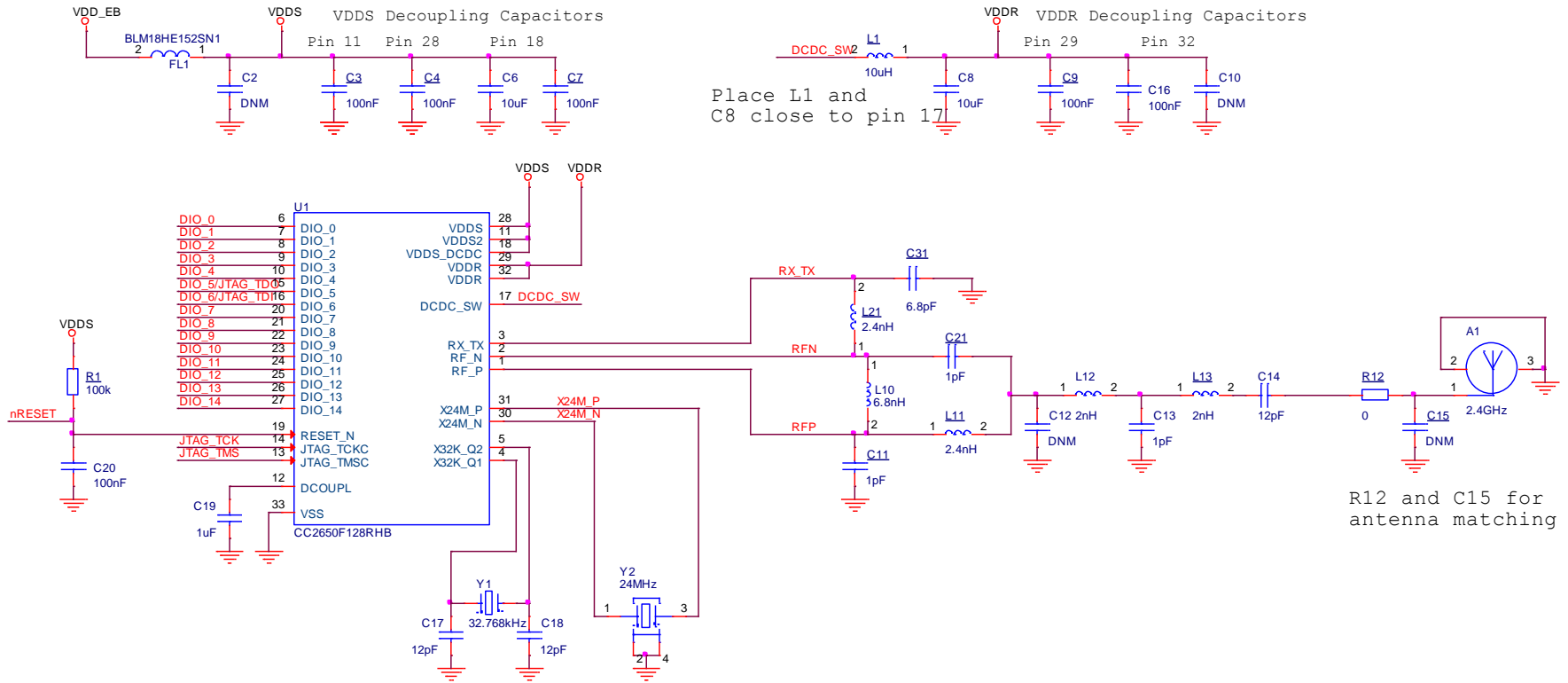


CC26xx HW Training

RF Front End options and Antennas

Fredrik Kervel, Bluetooth Smart Applications

Reference Schematic



Place L1 and C8 close to pin 17

R12 and C15 for antenna matching

RF pins


RF_P: RF positive output / input

RF_N: RF negative output / input

RX_TX: Optional RF bias pin

Several options on output configuration:

- Differential output: Both RF pins are used and a balun + a pi-filter is required between the CC26xx and the antenna
- Single ended output: Only one of the RF pins is used for RF output. Only a pi-filter is required between the CC26xx and the antenna. Output power is reduced and sensitivity is degraded
- External biasing of the RF pins can be applied through the RX_TX pin. This will improve sensitivity, but requires an additional inductor.
- For single ended configuration, the unused RF pin may alternatively be used as bias pin
- RX_TX can be used for external control of for example an RF switch

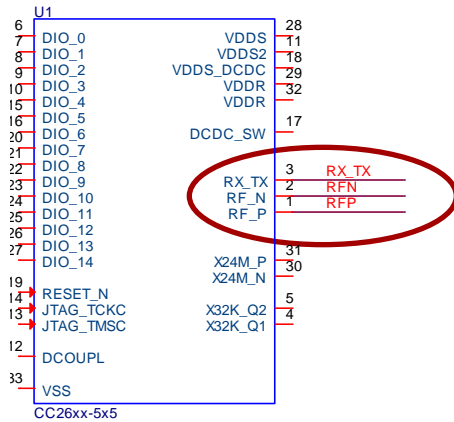


Note:


- The CC26xx 7x7 package does not have RX_TX-pin, while the CC13xx 7x7 package does.

RF Frontend options


External bias

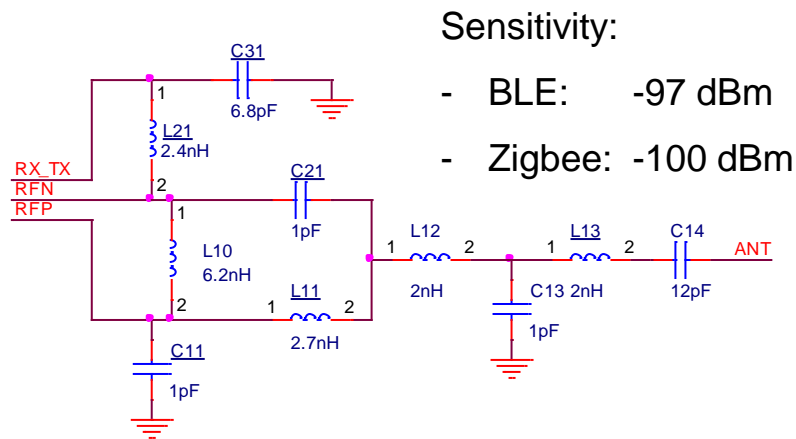


Sensitivity:

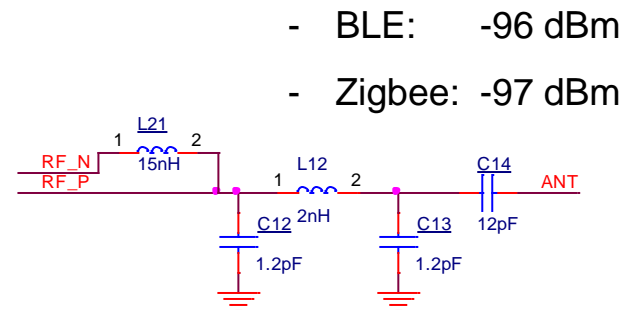

Internal bias

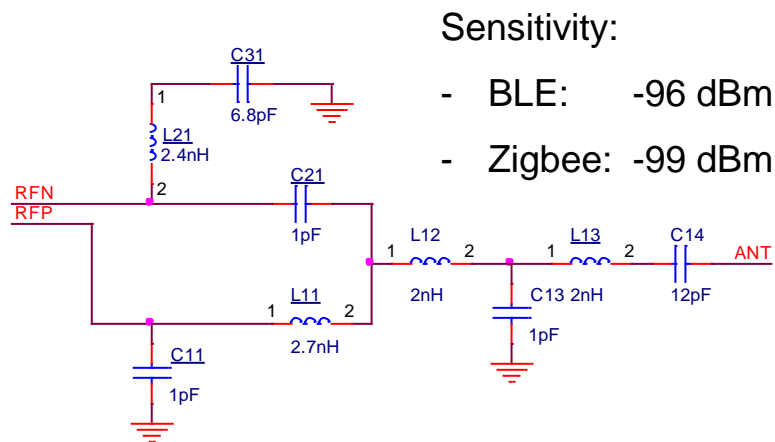

Sensitivity:

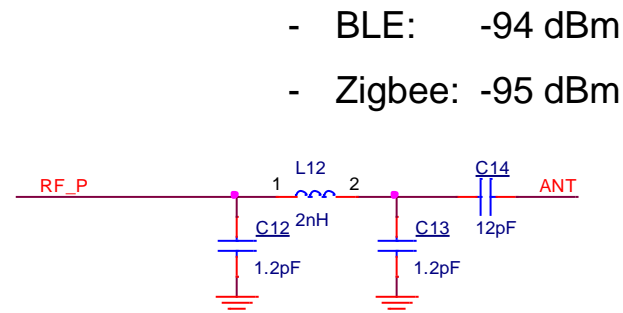

Pout_max = 5 dBm

Differential output


Pout_max = 2 dBm

Single-ended output


RF Frontend options

	Differential		Single Ended		
	Ext. Bias	Int. Bias	Ext. Bias	Int. Bias	
Output Power	5	5	2	2	[dBm]
BLE Sensitivity	-97	-96	-96	-94	[dBm]
Zigbee Sensitivity	-100	-99	-97	-95	[dBm]
Inductors	5	4	2	1	
Capacitors	5	5	3	3	
	10	9	5	4	

Antennas for 2.4 GHz

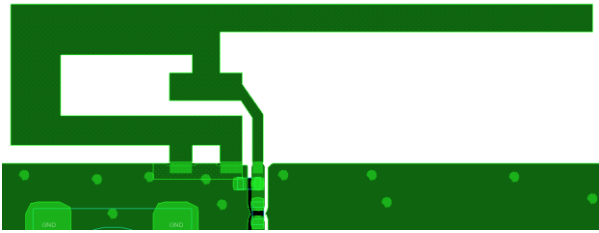

DN007

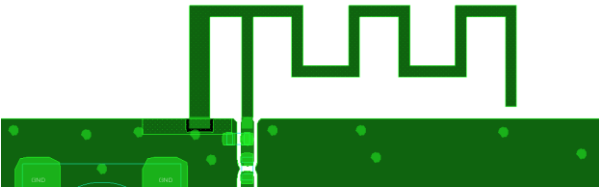

AN043

- PCB antennas
 - Low (no) cost
 - Simple to integrate (follow the reference design ☺)
 - Good performance
 - TI reference design for two different sizes which typically fits within customer requirements (board space), DN007 and AN043
 - Application Notes:
 - DN007: <http://www.ti.com/litv/pdf/swru120b>
 - AN043: <http://www.ti.com/litv/pdf/swra117d>
 - Antenna selection guide: <http://www.ti.com/litv/pdf/swra161b>
- Chip antennas
 - Can be used in applications where size is critical
 - Performance is comparable to PCB antennas (depending on size)
 - Cost is (obviously) higher
 - Contact antenna manufacturer for recommendations
 - Johanson, TDK, etc.
- Antenna tuning
 - Required for both PCB- and chip antennas
 - Can be done with matching network.....
 - or Antenna length (PCB antennas)

Available reference designs

- CC2650EM-7ID (7x7, Internal bias, Differential output)
- CC2650EM-5XD (5x5, External bias, Differential output)
- CC2650EM-4XS (4x4, External bias, Single ended output)
- CC2650EM-Murbal (5x5, Internal bias, Integrated balun)